

Electrical Engineering

ANALOG ELECTRONIC CIRCUITS (EE)

1. Design a suitable circuit to obtain the output level clipped at +3V and -4V for a 10V peak to peak sinusoidal input voltage.
2. What are the factors affecting stability of operating point of a transistor?
3. Draw and explain high frequency hybrid pi model of common emitter transistor.
4. What are the different topologies of feedback amplifiers?
5. What are the properties of an ideal opamp?
6. State Barkhausen criteria for sinusoidal oscillators.
7. With the help of a circuit diagram show how an opamp is used to get an output as $V_o = V_1 + V_2 - V_3 - V_4$, Where V_1, V_2, V_3 and V_4 are inputs to opamp.
8. Design an integrator that can integrate a square wave of peak-to-peak voltage 10V and frequency 1 kHz and draw the output waveform.
9. Explain the operation of a square waveform generator using opamp.
10. Design a Wein bridge oscillator to generate a sinusoidal waveform of 1 kHz.
11. Design a voltage divider bias circuit for a NPN transistor with $h_{fe} = 100$ and $V_{BE} = 0.6$ V, to operate from a 12 V dc supply. The bias conditions are $V_{ce} = 6$ V, $V_e = 1.2$ V and $I_c = 2$ mA.
12. Explain any one compensation technique used for reducing the drift of operating point.
13. Draw the h parameter model of a transistor in CE configuration. Also derive the expression for input impedance, current gain and voltage gain.
14. h-parameters of a transistor connected in CE configuration is $h_{ie} = 1000 \Omega$, $h_{re} = 10 \times 10^{-4}$; $h_{fe} = 50$; $h_{oe} = 100 \times 10^{-6} \Omega$. If the load resistance R_L is 1 K Ω , find:
 - i) The input impedance
 - ii) Current gain
 - iii) Voltage gain
15. Explain the working and characteristics of a N channel MOSFET.
16. Draw the frequency response of an amplifier. What is the significance of gain bandwidth product?
17. What is harmonics distortion in power amplifier? Discuss the operation of a class B power amplifier and derive its maximum power conversion efficiency.
18. Explain the working of a two stage RC coupled amplifier with circuit diagram.

19. Derive the expression for the voltage gain of an opamp based non-inverting amplifier.
20. Derive the frequency of oscillation of a RC phase shift oscillator using transistor.
21. Write short notes on the following:
 - i) CMRR
 - ii) Slew rate
22. Explain the operation of Hartley oscillator with a circuit diagram.
23. Draw and explain the operation of logarithmic amplifier.
24. What is the significance of UTP and LTP in Schmitt trigger circuits? Why is it called as regenerative comparator?
25. What are the features of instrumentation amplifier? Derive the expression for output voltage of an instrumentation amplifier.
26. Draw and explain the operation of a Triangular waveform generator using opamp
27. With the help of internal circuit diagram of IC555 explain the operation of a monostable multivibrator.
28. Design an astable multivibrator using 555 timers to generate an output signal with frequency 5 kHz and 50% duty cycle.